 


Maven Lab 2

1) Operators


CODE: SUM

```
module sum(input [3:0]a,input [3:0]b,output [3:0]result);  
assign result=a+b;  
endmodule  
NETLIST:
```




CODE: SUBTRACTOR
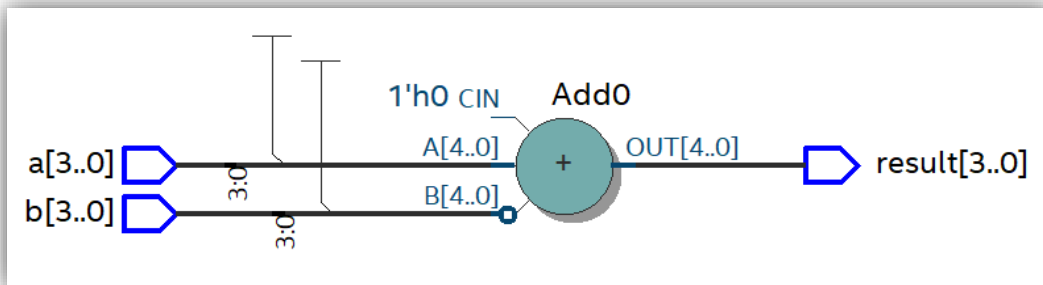
```
module sub(input [3:0]a,input [3:0]b,output [3:0]result);  
assign result=a-b;  
endmodule  
NETLIST:
```




CODE: MULTIPLICATION
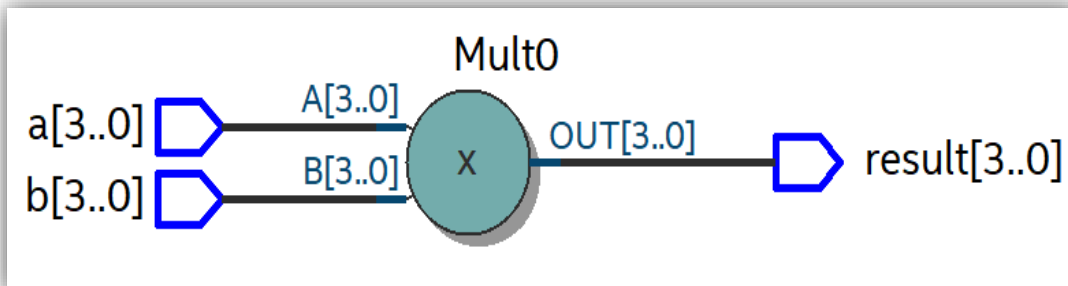
```
module mul(input [3:0]a,input [3:0]b,output [3:0]result);  
assign result=a*b;  
endmodule  
NETLIST:
```




CODE: DIVISION
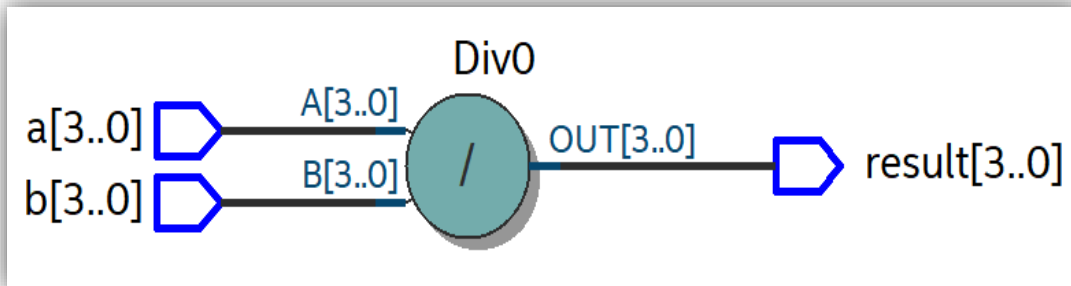
```
module div(input [3:0]a,input [3:0]b,output [3:0]result);  
assign result=a/b;  
endmodule  
NETLIST:
```




CODE: AND
 
```
module and_gate(input a,input b,output result);  
assign result=a&b;  
endmodule  
NETLIST:
```




CODE: OR

```
module or_gate(input a,input b,output result);  
assign result=a|b;  
endmodule  
NETLIST:
```

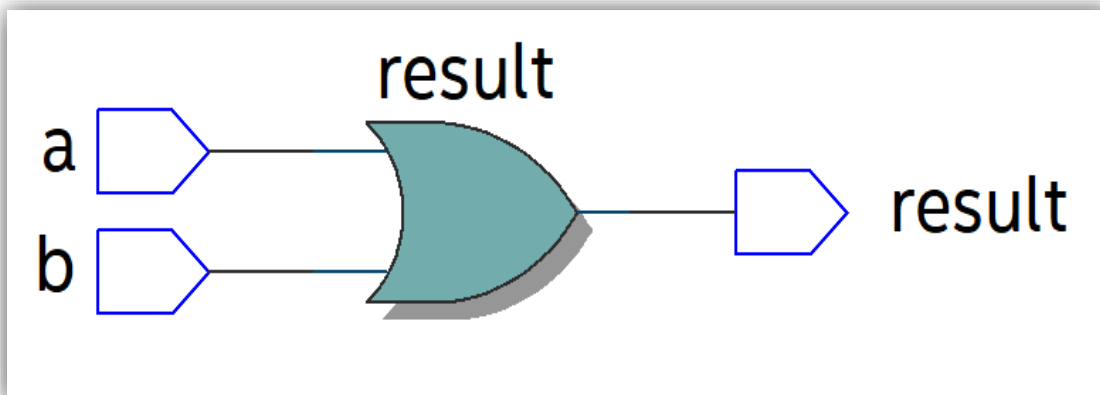


CODE: XOR
 
```
module xor_gate(input a,input b,output result);  
assign result=a^b;  
endmodule  
NETLIST:
```




CODE: EQUAL
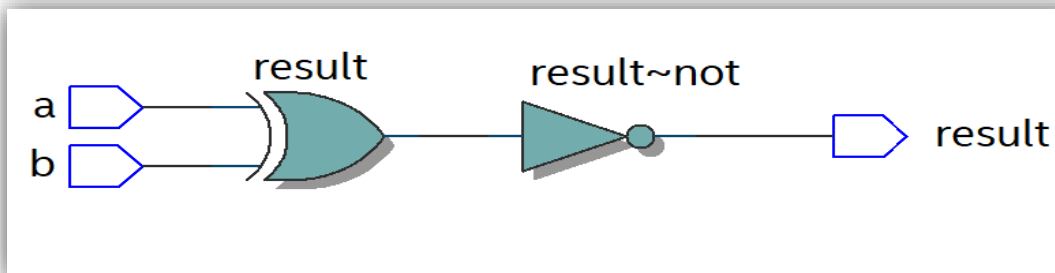
```
module equal_op(input a,input b,output result);  
assign result=(a==b);  
endmodule  
NETLIST:
```




CODE: EQUAL
 
```
module equal_op(input a,input b,output result);  
assign result=(a==b);  
endmodule  
NETLIST:
```




CODE:LEFT SHIFT
 
```
module Left_Shift ( input [3:0] data, output [7:0] result);  
assign result = data << 2;  
endmodule  
NETLIST:
```




CODE:RIGHT SHIFT
 
```
module Right_Shift ( input [3:0] data, output [7:0] result);  
assign result = data >> 2;  
endmodule  
NETLIST:
```



CODE:CONDITION OPERATOR

 
```
module Conditional_Op( input condition,input true_result,input false_result,output result);  
assign result = (condition) ? true_result : false_result;  
endmodule
```




2) ALU

CODE:

```
module ALU(input [7:0]a,input [7:0]b,input [2:0]opcode,input clk,input rst,output reg [7:0]result);
always@(posedge clk)
    begin
        if(rst)
            begin
                result=8'b0;
            end
        else
            begin
                case(opcode)
                    3'b000: result<=a+b;
                    3'b001: result<=a-b;
                    3'b010: result<=a*b;
                    3'b011: result<=a/b;
                    3'b100: result<=a&b;
                    3'b101: result<=a|b;
                    3'b110: result<=a^b;
                    3'b111: result<=(a>b)?8'b1:8'b0;
                endcase
            end
        end
    end
endmodule
```

 

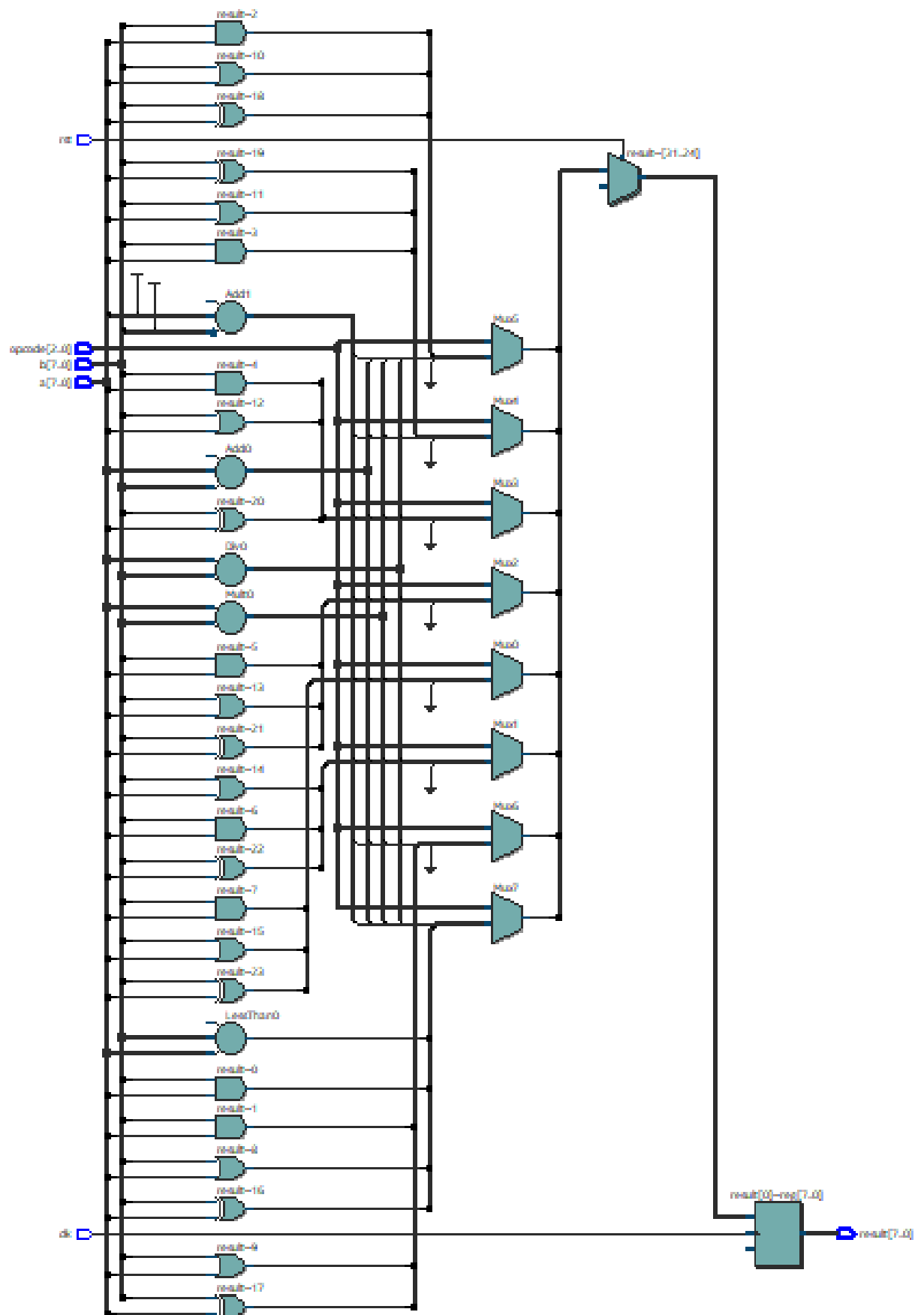

TESTBENCH:

```

module ALU_tb;
reg [7:0]a;
reg [7:0]b;
reg [2:0]opcode;
reg clk,rst;
wire [7:0]result;
integer i;
ALU dut(a,b,opcode,clk,rst,result);
initial
    begin
        a=8'b01100011;
        b=8'b00011001;
        clk=0;
        rst=0;
        opcode=8'b0;
    end
always
    begin
        #5 clk=~clk;
    end
initial
    begin
        rst=1;
        #10 rst=0;
        for(i=0;i<8;i=i+1)
            begin
                opcode = i;
                #10;
            end
        end
    end
endmodule

```

